

B. N. Bandodkar College of Science, Thane

First Term Examination, October, 2011
B. N. Bandodkar College of Science, Thane.

S. Y. B. Sc.

PHYSICS : PAPER – II

Duration : 2 Hours]

[Marks : 60

- N.B. (1) All questions are compulsory.
(2) Figures to the right indicate full marks.
(3) Use of non programmable calculator is allowed.

1. (a) Attempt any **THREE** of the following: 12
- i) Explain the working of velocity selector
 - ii) An electron is accelerated from rest by a potential difference of 2000 volts; calculate the velocity acquired by electron.
($e = 1.6 \times 10^{-19} \text{ C}$; $m_e = 9.1 \times 10^{-31} \text{ kg}$)
 - iii) State why silicon devices are preferred over germanium devices.
 - iv) Explain how negative feedback can increase the value of the bandwidth of an amplifier.
 - v) Convert Binary to Decimal using Double-dable method -101011
- (b) Add the following binary numbers 3
- $$\begin{array}{r} 1011101 \\ + \\ 0111010 \end{array}$$
2. (a) Attempt any **ONE** of the following: 8
- i) For the motion of a charge particle 'q' having mass 'm' in sinusoidal electric field $E = E_0 \sin \omega t$, obtain the expressions for acceleration, velocity and displacement.
 - ii) Explain the construction and working of Cyclotron.
- (b) An electron is revolving in a magnetic field of 10^{-4} Wb/m^2 acting 4
perpendicular to the plane of its path. Find the frequency of revolution.
($e = 1.6 \times 10^{-19} \text{ C}$; $m_e = 9.1 \times 10^{-31} \text{ kg}$)
- (c) Show that the kinetic energy of a charge particle remains constant in 3
magnetic field.

P.T.O.

3. (a) Attempt any **ONE** of the following: 8
- i) Explain how mid-point biasing provides best possible ac amplification from the transistor circuit.
- ii) What is feedback in amplifier. Derive the relation between the gain without feedback and gain with feedback when negative feedback is introduced.
- (b) For a voltage divider bias circuit $R_1= 6k\Omega$, $R_2= 4k\Omega$, $R_c=R_e=5k\Omega$, $\beta=100$ and $V_{cc}=30V$ determine V_{Th} , R_{Th} , I_c , I_b 4
- (c) An amplifier has the following characteristics $R_i=2.5k\Omega$, $R_o=50k\Omega$ and $A_v=100$. If **3%** negative voltage feedback in series with the input is used, determine its voltage gain. 3
4. (a) Attempt any **ONE** of the following: 8
- i) Explain Sum of products (**SOP**) using 3 inputs.
- ii) Draw the logic circuit of an **RS** flip flop using **NAND** gates. Write down its state transition table.
- (b) Convert the following numerical form into sum of the product form $f(A,B,C)= \sum m(0,1,7)$ 4
- (c) Explain the terms ‘Up counter’ and ‘Down counter’. 3

~~*~*~*~*~*~*~*~*~*~*~*~*~*~*