

B. N. BANDODKAR COLLEGE OF SCIENCE, THANE

F.Y.B.Sc. - A.T.K.T. AUG.2011

PHYSICS-II

MARKS : 90

- N.B.:** 1) All questions are **compulsory**.
2) Figures on the right indicate **full marks**.
3) **Non – programmable calculators** are allowed.

SECTION: I

- Q.1) (A)** Answer any **ONE** of the following. **(8)**
- (a) A source of constant e.m.f. is connected across a series combination of a capacitor and a resistance. Derive an expression for the charge on the capacitor and current through the circuit during charging.
- (b) What is a transformer? What are step-up and step-down transformers?
Show that , for an ideal transformer $\frac{V_2}{V_1} = \frac{I_1}{I_2} = \frac{N_2}{N_1}$.
- (B)** Draw a neat labeled Resonance Curve for series LCR circuit and write the formula for resonant frequency. **(4)**
- (C)** A 0.1 H inductance is connected across an ac supply of r.m.s. e.m.f. 25 V and frequency 1 kHz. Neglecting the resistance of the inductor, calculate the r.m.s. current flowing through it. **(3)**
- Q.2) (A)** Answer any **ONE** of the following. **(8)**
- (a) State Bohr's first and second postulates of nuclear model of atom and hence obtain an expression for radius of a stationary orbit around the nucleus of charge Ze. Calculate the Bohr radius.
- (b) State five important properties of X rays. Explain production of X rays. Write experimental observations.
- (B)** Explain : i) Emission spectra
ii) Absorption spectra **(4)**
- (C)** An X ray tube emits X rays with minimum wavelength 0.1 \AA . What is the operating voltage of the tube? **(3)**
- Q.3) (A)** Answer any **ONE** of the following. **(8)**
- (a) What is a transistor? What are its three configurations of operation? Draw a neat labelled circuit diagram
(i) to study characteristics of NPN transistor in CE mode.
(ii) of Darlington pair of NPN transistors.
- (b) Describe NAND gate as a universal building block with logic diagrams and truth tables.
- (B)** Define current amplification factor α and β . Show that $\beta = \frac{\alpha}{1-\alpha}$. **(4)**
- (C)** Draw the logic diagram of the following equation,
 $(\bar{A} + B) \bar{A} \cdot \bar{B} \cdot \bar{C} = \overline{A + B + C}$ **(3)**

SECTION -II

- Q.4 (A)** Answer any **ONE** of the following. (8)
- (a) State and prove Maximum Power Transfer Theorem.
 - (b) Obtain the balance condition for Wien bridge with a neat circuit diagram. How would you determine the frequency of the ac supply?
- (B)** A B.G. has current sensitivity of $500 \text{ mm}/\mu\text{A}$. Find the current that produces a deflection of 1 mm. The coil has period 6 second, What is the charge sensitivity? (4)
- (C)** Define the following: (3)
- (i) Charge sensitivity
 - (ii) Figure of merit
 - (iii) Norton Theorem
- Q.5 (A)** Answer any **ONE** of the following. (8)
- (a) State and explain the properties of a nucleus.
 - (b) Explain the following induced transformations of atomic nuclei:
(i) α - decay (ii) β - decay (iii) γ - decay
- (B)** If a sample of radium has half life time of the order 22 years, find the time taken by sample to decrease to 10 %. (4)
- (C)** What is atomic mass unit? Show that $1 \text{ a.m.u.} = 931 \text{ MeV}$ (3)
- Q.6 (A)** Answer any **ONE** of the following. (8)
- (a) Explain Compton effect and show that the Compton Shift is
$$\Delta\lambda = \frac{h}{m_0 c} (1 - \cos\theta)$$
 - (b) With the help of a neat labeled diagram, explain the set up of Davisson-Germer on electron diffraction.
- (B)** State de-Broglie hypothesis and mention 4 characteristics of Matter Waves. (4)
- (C)** What is the de-Broglie wavelength associated with a proton moving with a velocity equal to $(1/30)^{\text{th}}$ the velocity of light. (3)
[$m_p = 1.67 \times 10^{-27} \text{ kg}$]

~~*~*~*~*~*~*~*~*